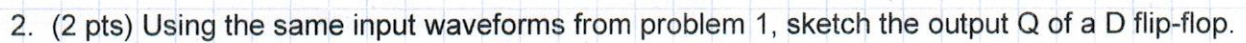


Name: ZACH D'AGOSTINO

CLK / EN





3. For both flip-flops in the circuit below, the setup time is 1nsec, the hold time is 0nsec, and the propagation delay is 10nsec.

