

Homework 5 (Problem 2 on other side!)

1. Design a counter to produce the following binary sequence (use D flip-flops): 9, 12, 11, 13, 15, 14, 10, 9,...

8 4 2 1


Q_3, Q_2, Q_1, Q_0

1	0	0	1	= 9
1	1	0	0	= 12
1	0	1	1	= 11
1	1	0	1	= 13
1	1	1	1	= 15
1	1	1	0	= 14
1	0	1	0	= 10
1	0	0	1	= 9

Q_3, Q_2, Q_1, Q_0 Q_2, Q_1, Q_0

0	0	0	→	X	X	X
0	0	1	→	1	0	0
0	1	0	→	0	0	1
0	1	1	→	1	0	1
1	0	0	→	0	1	1
1	0	1	→	1	1	1
1	1	0	→	0	1	0
1	1	1	→	1	1	0

D_2, D_1, D_0

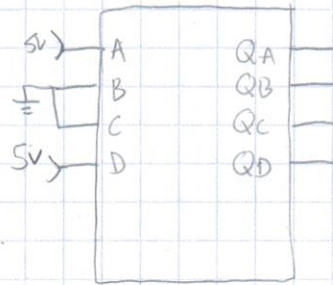

K-MAP

Q_2, Q_1	Q_0, Q_0
Q_2, Q_1	X 1
Q_2, Q_1	1 1
Q_2, Q_1	1 1
Q_2, Q_1	1 1

Q_2, Q_1	Q_0, Q_0
Q_2, Q_1	X 1
Q_2, Q_1	1 1
Q_2, Q_1	1 1
Q_2, Q_1	1 1


Q_2, Q_1	Q_0, Q_0
Q_2, Q_1	X 1
Q_2, Q_1	1 1
Q_2, Q_1	1 1
Q_2, Q_1	1 1

$$D_2 = Q_0$$

$$D_1 = Q_2$$

$$D_0 = \overline{Q_2} Q_1 + Q_2 \overline{Q_1}$$

$$D_0 = Q_2 \oplus Q_1$$

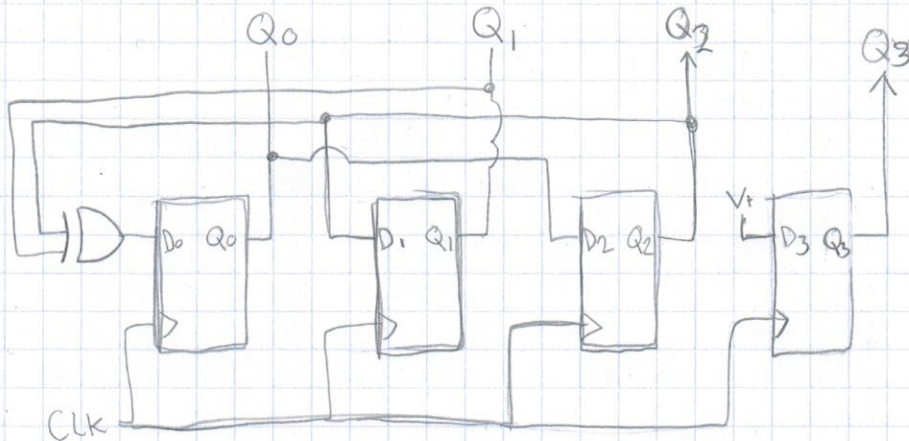

2. Design a Mealy circuit to find the pattern ...11011... in a series of binary numbers, where each new bit appears on the input to the circuit with each clock pulse. An output should be switched to high when the last number in the pattern is detected. Allow overlapping patterns.

11011


5 STATES →

any input to get to 101

1 1 0 1 1 0

4 STATES

	Q_2	Q_1	Q_0	A
0	0	0	0	
1	0	0	1	
2	0	1	0	
3	0	1	1	
4	1	0	0	

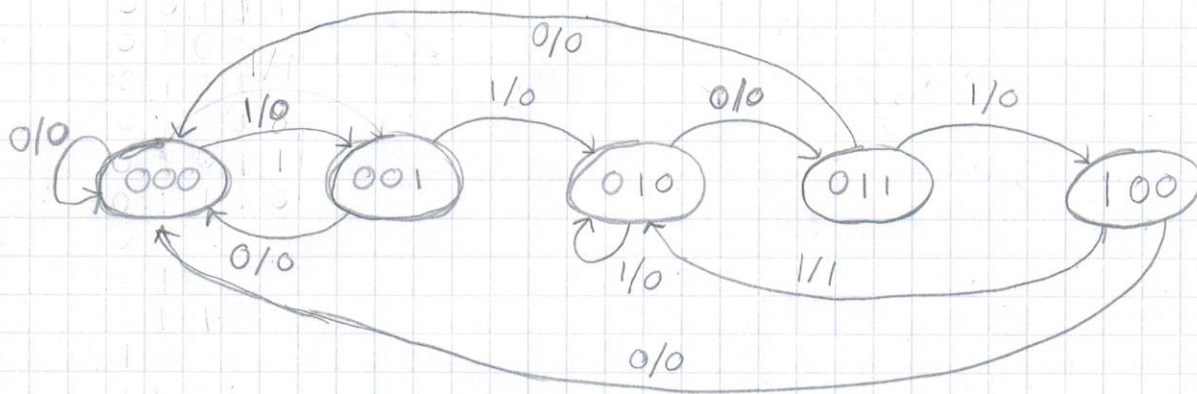

$$D_0 \rightarrow Q_2 \bar{Q}_0 A + Q_2 Q_1$$

$$D_1 \rightarrow Q_1 \bar{Q}_0 + Q_2 A + \bar{Q}_1 Q_0 A$$

$Q_2 Q_1$	$Q_0 A$	$\bar{Q}_0 A$	$Q_0 A$	$Q_0 A$
00	0	1	0	0
01	1	0	0	0
10	X	X	X	X
11	0	0	X	X

$Q_2 Q_1$	$\bar{Q}_0 A$	$Q_0 A$	$Q_0 A$	$Q_0 A$
00	0	0	1	1
01	1	1	1	1
10	X	X	X	X
11	X	X	X	X

$Q_2 Q_1 Q_0$	In	$Q_2 Q_1 Q_0$	Out
000	0	000	0
000	1	001	0
001	0	000	0
001	1	010	0
010	0	010	0
010	1	011	0
011	0	000	0
011	1	100	0
100	0	000	0
100	1	010	1
101	0	X X X	
101	1	X X X	
110	0	X X X	
110	1	X X X	
111	0	X X X	
111	1	X X X	

$$D_2 \rightarrow Q_1 \bar{Q}_0 A$$

$$\text{Output} \rightarrow Q_2 \bar{Q}_1 \bar{Q}_0 A$$

$Q_2 Q_1$	$Q_0 A$	$\bar{Q}_0 A$	$Q_0 A$	$Q_0 A$
00	0	1	0	0
01	1	0	0	0
10	X	X	X	X
11	0	0	X	X

$Q_2 Q_1$	$\bar{Q}_0 A$	$Q_0 A$	$Q_0 A$	$Q_0 A$
00	0	0	1	1
01	1	1	1	1
10	X	X	X	X
11	X	X	X	X