

Assignment 2

Schoelen EET122, Spring 2020 Remote

RevB: 04/09/2020

Contents

Week2: Start 04/09/20 - End 04/16/20	1
Objectives:	1
Read / Watch:	2
Do:.....	2
Deliverables to be uploaded to D2L for grading	2
Appendix	3
Breadboard Sketch.....	3
Kicad.....	3
Place Component	3
Annotate	6

Week2: Start 04/09/20 - End 04/16/20

Objectives:

1. Gain familiarity with Ki Cad schematic capture by doing a few simple KiCad tasks
2. Continue to gain knowledge of circuits by building and debugging.
3. Exposure to synchronous circuits (flip-flops, yeah!)
4. Gain familiarity with Arduino IDE by performing a simple task.

Read / Watch:

Last week's links if you need a review.

Do:

Use the Lab2 Discussion board if you need help.

See Appendix for additional details

1. Load into KiCad: EET122_Lab2 from D2L
2. Complete the schematic using week1 schematic as a reference
 - a. Add the 74ls74
 - b. Add the two leds and two resistors
 - c. Set the value of the resistors to 1k
 - d. Annotate the design so that all components have a reference designator.
3. Complete the truth table in section A3 of the schematic
4. Do a sketch of your breadboard layout before you build
5. Be sure your UNO has the sketch loaded from Lab1
6. Build the circuit on a breadboard and connect to the Arduino as shown in the schematic (Based on the truth table derived in item #3 you should be able to know if your circuit is operating correctly).
7. Once you have the circuit working, open the Arduino IDE and load sketch from week. At the top of the program is a #define that sets the clock time high and time low (in milli-seconds). Change the #define to 50. Program it into the UNO.


Deliverables to be uploaded to D2L for grading

For the deliverable use this naming convention please: LastNameFirstName_L2

1. Upload the KiCad files, both the .pro and the .sch
2. Shoot a video of your circuit with LEDs blinking at the rate dictated by the new #define we did in item #7 above. Upload to D2L deliverables for lab2.
3. Scan or shoot a picture of your pre-layout sketch (item #4 above)
4. Document a conclusion. The conclusion is free form, it's a reflection on the lab. There's no minimum length. What you write is completely up to you. Upload conclusion to D2L deliverables Lab2. Some topics you cover may be:
 - a) What did you learn?
 - b) What did you struggle with?
 - c) What was too easy?
 - d) Observations if any
 - e) Comments if any
 - f) How many hours did this lab take you to complete (all the tasks)

Appendix

Breadboard Sketch

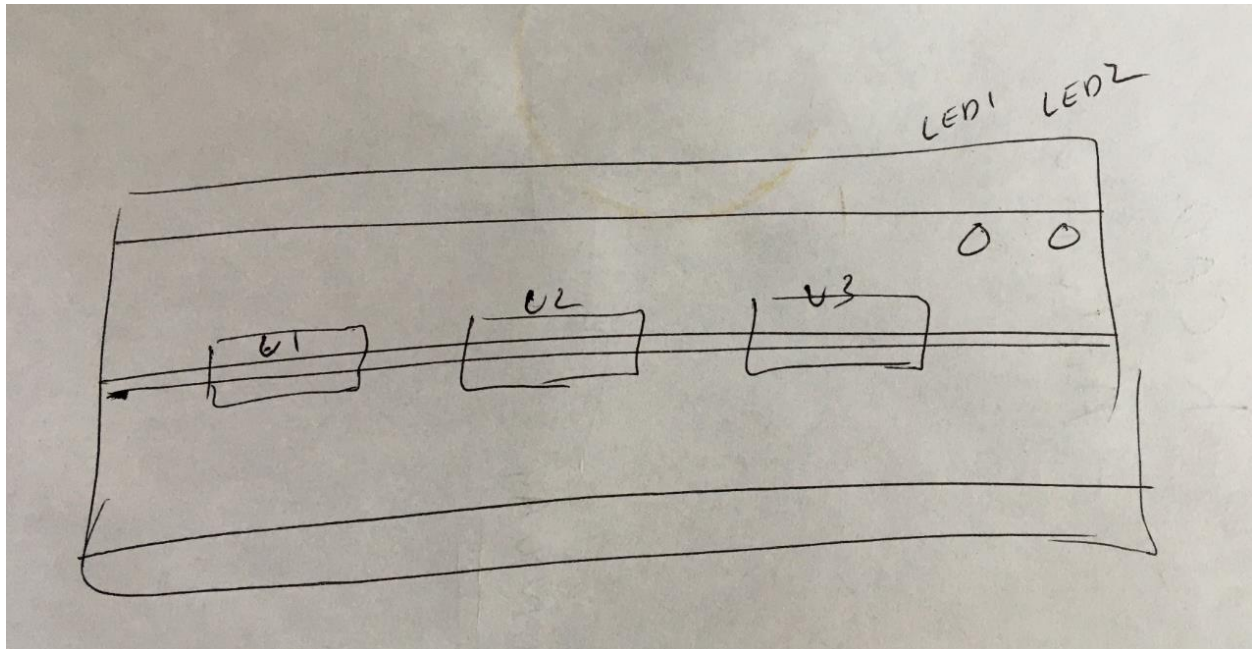


Kicad


Place Component

To place a component:

1. Click the Place Symbol Icon

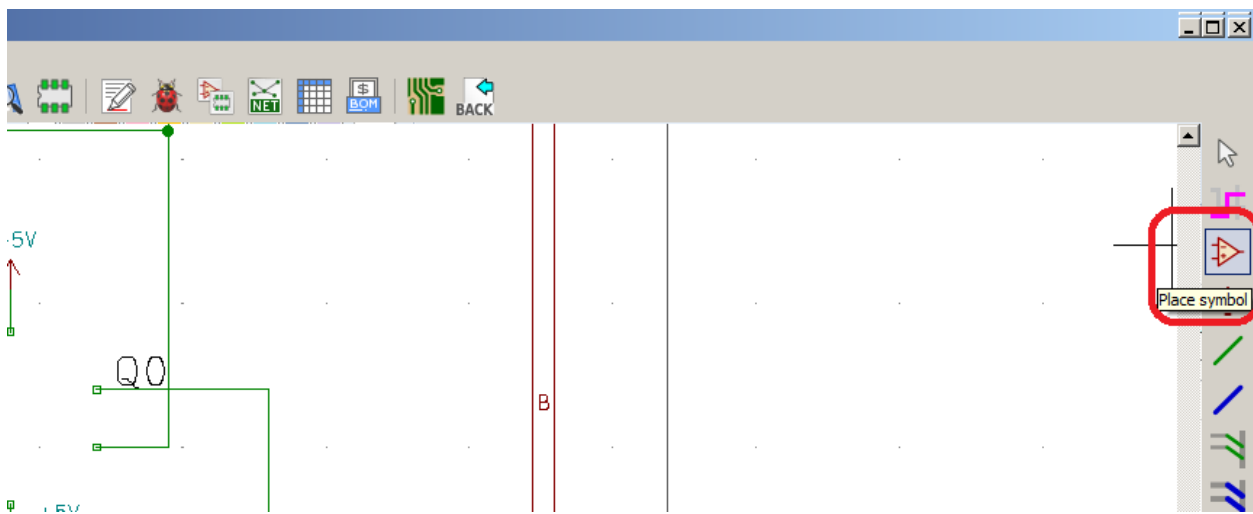

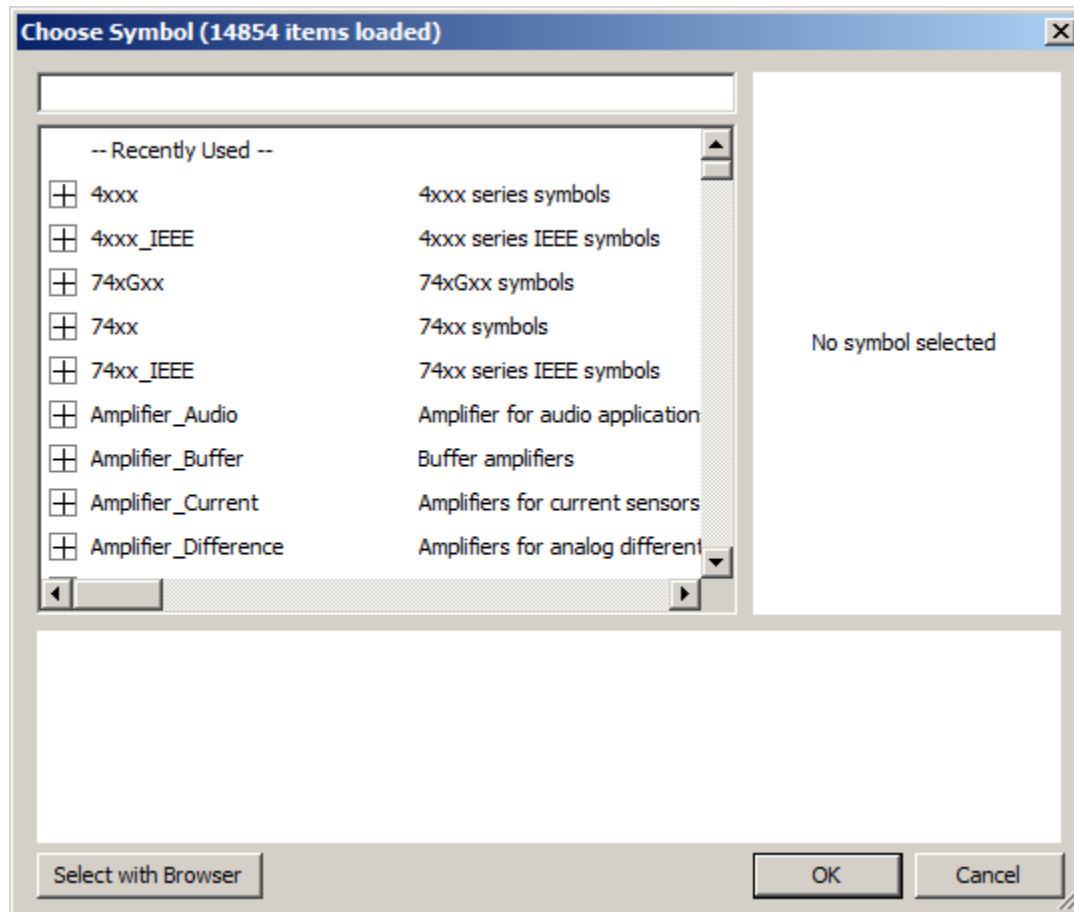
2. Click the workspace (a choose symbol box will open)




3. In filter type 74ls74

4. Expand the hierarchy to get to 74Ls74 Dual D Flip-Flop, Set & Reset

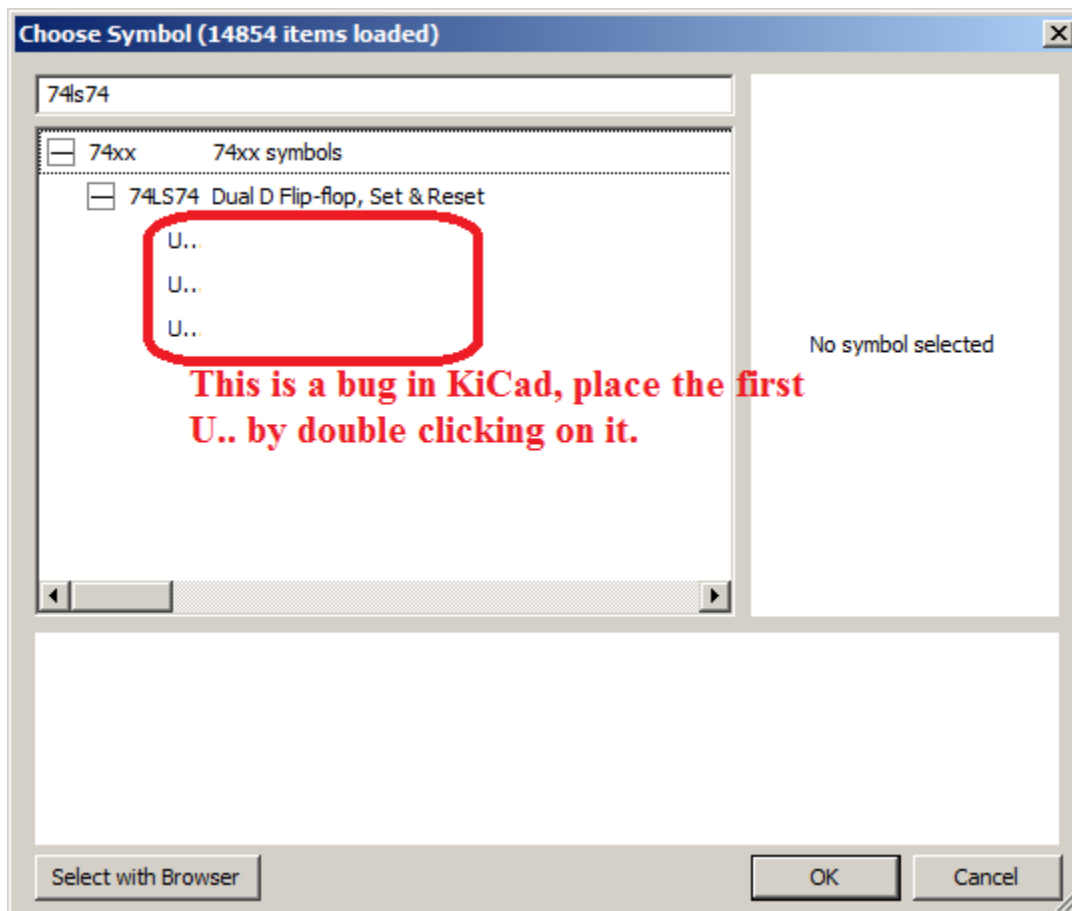5. Double click on the first U.. and place the component in the schematic.



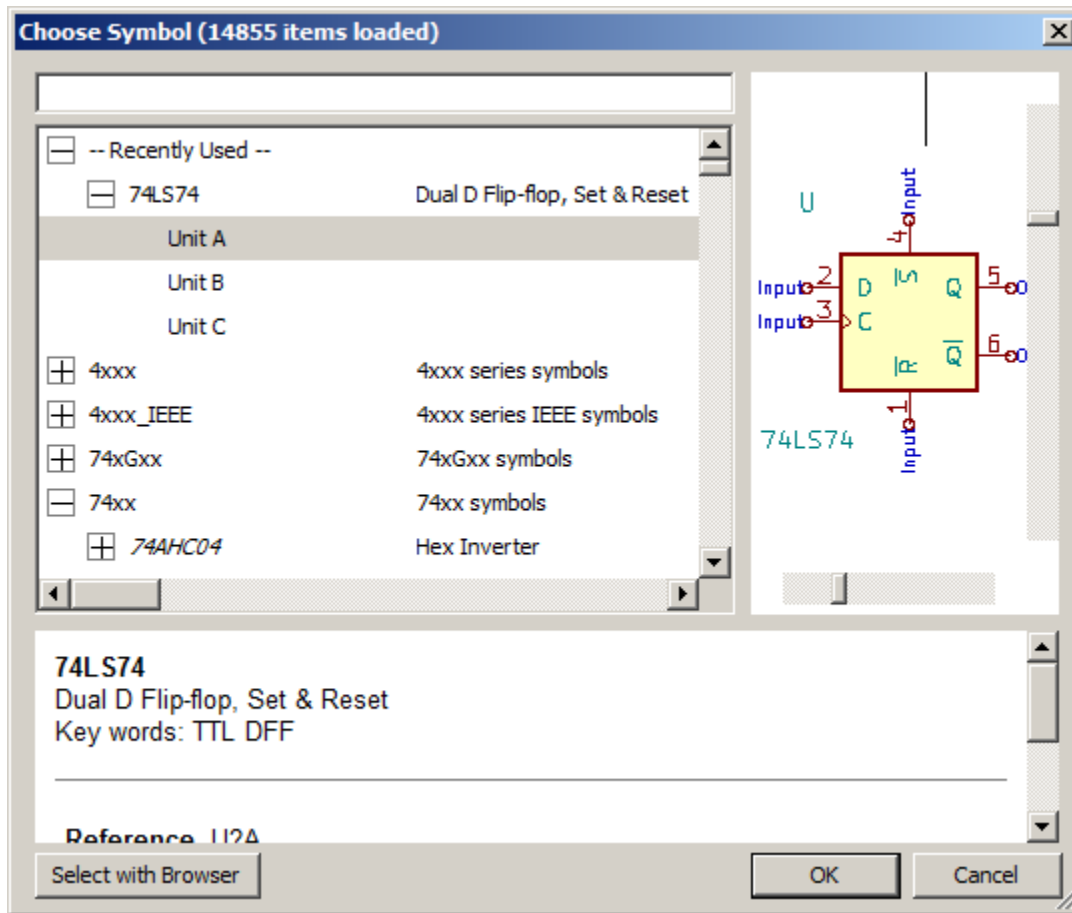6. Place the remaining two components (Unit B and Unit C) of the 74LS74 one at a time.



Annotate

To annotate the design (that is, to automatically assign reference designators) click the Annotate schematic symbols icon.

